

Title Page.

Mid-term Paper  
Electronic Circuit

Name: ASHFAQ AHMAD

Reg NO: 19PWCSE 1795

Reg:

Section: B

Answer No: 01

Given:

$$E = 7 \text{ Volt}$$

$$R = 1.54 \text{ k}\Omega$$

Required:

$$I_D = ?$$

$$V_D = ?$$

$$V_R = ?$$


Sol

$$I_D = E/R$$

$$I_D = 7 / 1.54 \times 10^3 \text{ A}$$

$$I_D = 4.55 \times 10^{-3} \text{ A}$$

$$\boxed{I_D = 4.55 \text{ mA}}$$

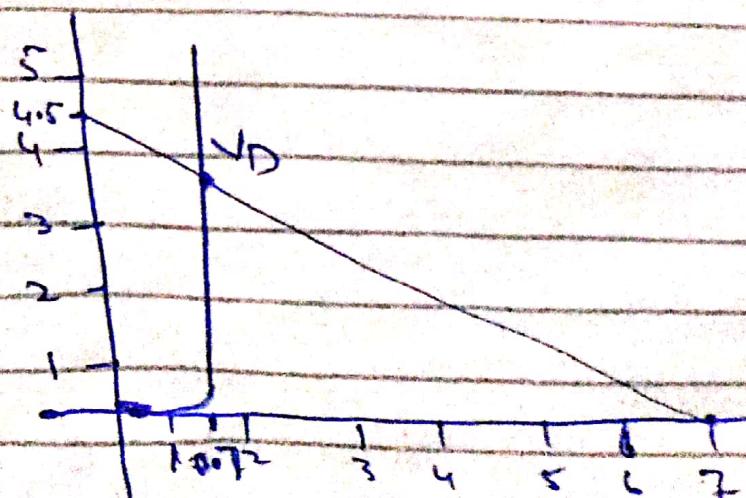

Page (3)

$$\underline{V_D} = -2V$$

Approximately:

$$\nabla R = ?$$

$$V_R = E - V_d$$

$$N_R = 7 - 2$$


$$V_R = 5 \text{ Volt}$$

Answer No : 02

Given:

$$E_1 = 15$$

$$E_2 = -9$$

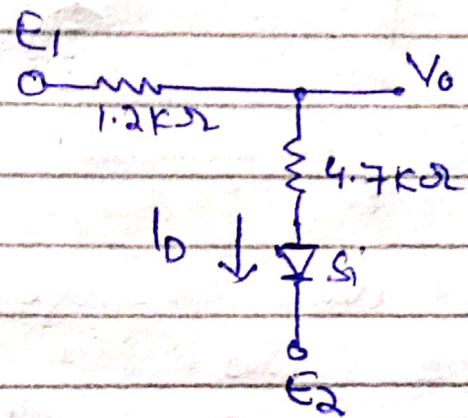

Required.


$$V_0 = ?$$

$$I_0 = ?$$

Sol

Now Redesign the circuit  
we will include 0.7V  
battery because of silicon  
diode

$$P = T + \alpha$$

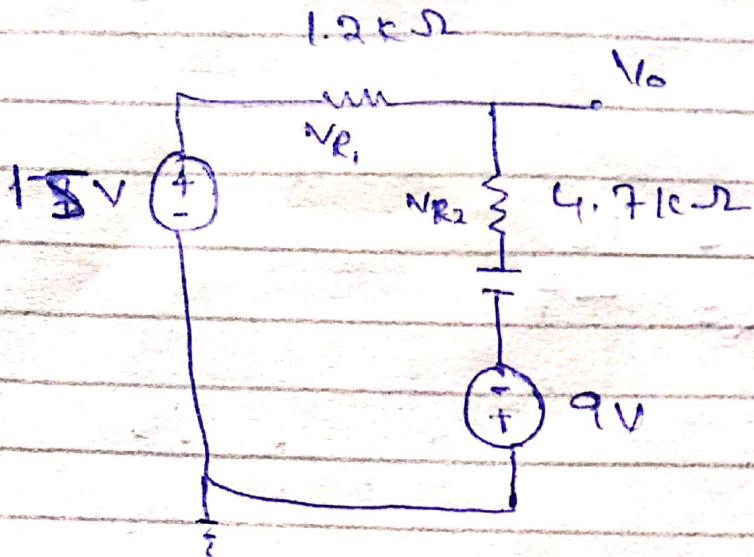

As we changed polarity of  
 $E_2$  so :

$$E_2 = +9V$$

Now apply KVL


$$15V - (1.2k\Omega) \times I_D - 4.7k\Omega \times I_D - 0.7V + 9V = 0$$

$$- [1.2k\Omega + 4.7k\Omega] I_D + 23.3V = 0$$

$$I_D = \left( \frac{23.3}{5.9k} \right) \text{mA}$$

$$I_D = 3.95 \text{ mA}$$

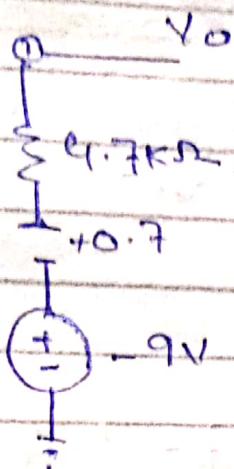Now  $V_o$  is the sum of  $E_2$ , the voltage across  $4.7\text{ k}\Omega$  resistor and  $V_d$  of Diode, so



here I again changed the polarity of  $E_2$ .

$$V_o = V_R + 0.7V + (-9V) = 0$$

$$V_R = I_D R = (3.95\text{ mA}) \times (4.7\text{ k}\Omega)$$

$$V_R = 18.57\text{ V}$$

$$V_o = 18.57 + 0.7 - 9$$

$$V_o = 10.27\text{ V}$$

Ans

— XX — XX — XX ✓

Answer NO: 03

Given:

$$V_i = 111$$


$$R = 1.6 \times 10^3 \Omega$$

(a)

$$V_{dc} = ?$$

Sol

Full-wave bridge Rectifier

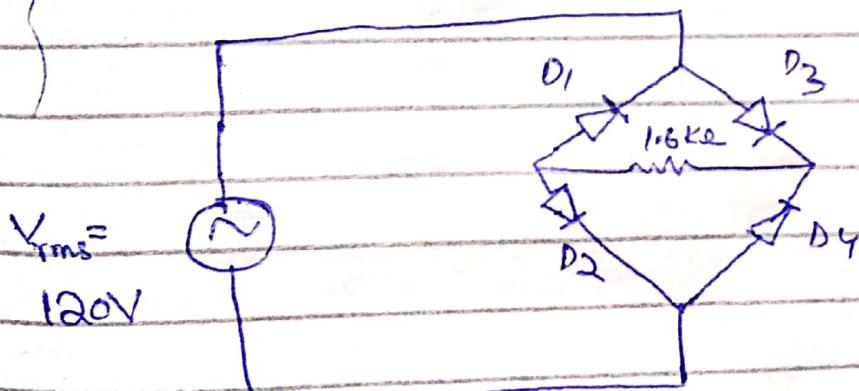

Now Peak voltage of  
if Input voltage is

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_m = \sqrt{2} V_{rms}$$

$$V_m = \sqrt{2} (111)$$

$$V_m = 157 \text{ V}$$

Now formula for finding  
 $I_{dc}$  is.

$$I_{dc} = 0.636 (V_m - 1.4 \text{ V})$$

Put values

$$I_{dc} = 0.636 (157 - 1.4)$$

$$I_{dc} = 98.9 \text{ V}$$

~~6 x ————— x x —————~~

$$(b) PIV_{\min} = ?$$

Step

formula for finding  
 $PIV_{\min} = V_m - V_K$

$V_K$  = Knee voltage of Diode  
 here Diode is Silicon  
 So for Silicon

$$V_K = 0.7 \text{ V}$$

$$P_{IV\min} = 157 - 0.7$$

$$P_{IV\min} = 156.3 \text{ A}$$

Now in milliAmpere,

$$\boxed{P_{IV\min} = 156300 \text{ mA}}$$

$$\text{C) } I_m = ?$$

Sol

Now formula for finding  $I_m$  is,

$$I_{max} = \frac{N_m - 1.4}{R}$$

Put values

$$I_m = \frac{157 - 1.4}{1.6 \times 10^3}$$

$$I_m = 97.25 \times 10^{-3} \text{ A}$$

$$\boxed{I_m = 97.25 \text{ mA}}$$

Ans

XX — XX — XX

# Answer No: 04

Given:

$$V_m = 143$$

$$\bar{E} = 6$$


Required:

$$V_c = ?$$


$$V_{o+} = ?$$

$$V_{o-} = ?$$

Sol

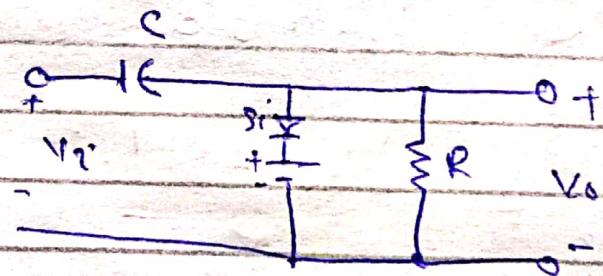

Input Signals are

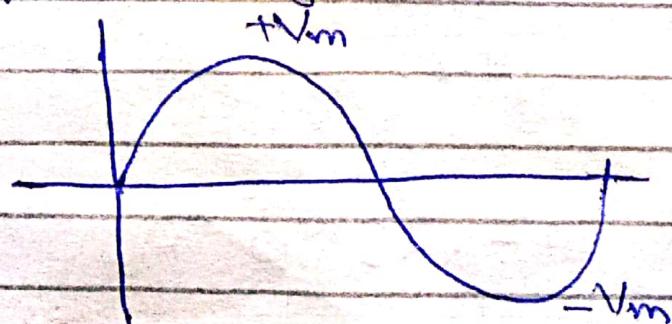

formula for  $V_c$  ie,

$$V_c = V_m - (E + 0.7)$$

$$V_c = 143 - (6 + 0.7)$$

$$V_c = 136.3 \text{ Volt}$$


Now  $V_o^+$  is given by,

$$V_o^+ = E + 0.7v$$

$$V_o^+ = 6 + 0.7v$$

$$V_o^+ = 6.7v$$

Output Signal

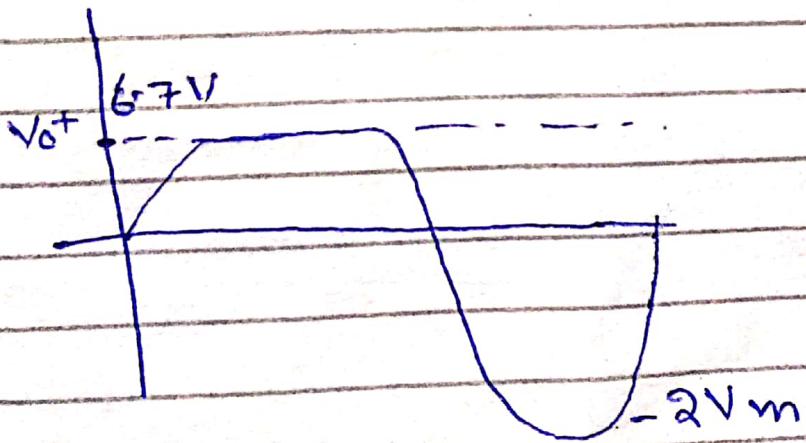

$V_o^-$  will reach to  $-2V_m$

so

$$V_o^- = -2V_m$$

$XX \longrightarrow Xb \checkmark Xo$

(11)

Answer  $NO = 5$

Given

$$R_s = 99 \Omega$$

$$V_2 = 14 V$$


$$R_L = 280 \Omega$$

Required:

$$V_{i\max} = ?$$

$$V_{i\min} = ?$$

Sol

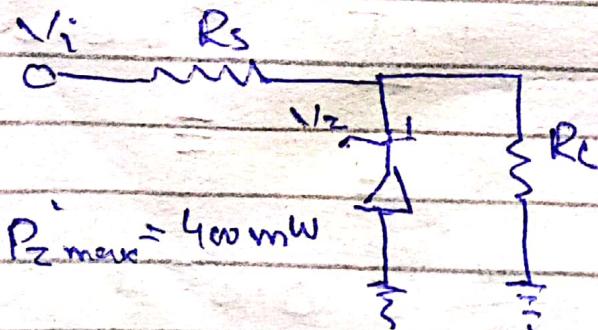

$$P_{2\max} = 400 mW$$

Now Voltage across  
diode should be  $14V$ .

Now we consider  $V_2$  as  
open circuit and apply  
[CV].

12

$$V_2 = \frac{14(99)}{28} + 14V =$$


$$V_2 = 4.9 + 14$$

$V_{2\text{mini}} = 18.9 \text{ V}$

Since  $P_{2\text{max}} = 400 \text{ mW}$   
and  $V_2 = 14V$

$$I_{2\text{max}} = \frac{400 \text{ mW}}{14V} =$$

$$I_{2\text{max}} = 28.57 \text{ mA}$$

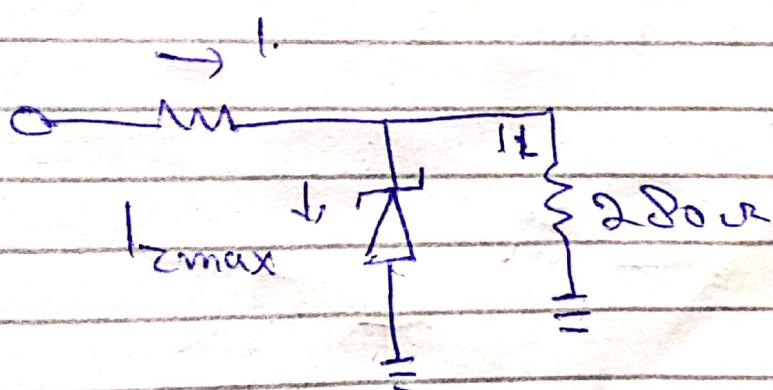

$$I_L = \frac{14}{280} = 0.05A$$

$$I_L = 50 \text{ mA}$$

$$I_{2\text{max}} = 28.57 \text{ mA}$$

P & T + O

(13)

$$\text{Now } I_{\max} = I_{z\max} + I_C$$

$$I_{\max} = 78.57 \text{ mA}$$

This is the current that should flow across R

$$I_{R_s} = \frac{V_i - 14V}{99}$$

$$I_{\max} = \frac{V_{imax} - 14V}{99.52}$$

$$\text{Put } I_{\max} = 78.57 \text{ mA}$$

$$78.57(99) + 14V = V_{imax}$$

$$V_{imax} = 7792.43 \text{ mV}$$

$$V_{imax} = 7.8V$$

$$V_{imin} = 18.9V$$

18

$$7.8 \leq V_i \leq 18.9V$$

$\times \text{ P } \times$  —  $\times \text{ P } \times$

The EMF